

Paola Andrea Campiño - Jose Gabriel Ruiz Bayer

# BIBLIOTECA DE COMPONENTES

**PUBLISHED BY UNIVERSIDAD DE LOS ANDES - COLOMBIA**



This work is licensed under a Creative Commons Attribution-NonCommercial-NoDerivatives 4.0 International License.

*September 2018*

# Contenido

<b>1</b>	<b>Diseño de componentes. ....</b>	<b>5</b>
<b>1.1</b>	<b>Neurona Artificial</b>	<b>5</b>
1.1.1	Descripción del componente .....	5
1.1.2	Símbolo .....	6
1.1.3	Diagrama caja negra .....	6
1.1.4	Funcionalidad .....	6
1.1.5	HDL: Caja negra .....	7
1.1.6	Definición vectores de prueba .....	8
1.1.7	HDL: Vectores de prueba .....	8
1.1.8	Diagrama caja blanca .....	10
1.1.9	HDL: Caja blanca .....	11
1.1.10	HDL: bloques .....	13
1.1.11	Simulación temporal .....	15
1.1.12	Diagramas QUARTUS .....	16
1.1.13	Resultados y lecciones aprendidas .....	17



## Neurona Artificial

Descripción del componente  
Símbolo  
Diagrama caja negra  
Funcionalidad  
HDL: Caja negra  
Definición vectores de prueba  
HDL: Vectores de prueba  
Diagrama caja blanca  
HDL: Caja blanca  
HDL: bloques  
Simulación temporal  
Diagramas QUARTUS  
Resultados y lecciones aprendidas

# 1. Diseño de componentes.

HENRY FORD

Si le hubiera preguntado a la gente lo que  
ellos querían, ellos habrían dicho caballos  
más rápidos.

## 1.1 Neurona Artificial

A continuación se presenta el componente combinacional **Neurona Artificial** mostrando su descripción con ecuación lógica.

### 1.1.1 Descripción del componente

#### A. Descripción de componente:


Una neurona artificial es uno de los elementos más simples que conforman las redes neuronales. Una neurona artificial puede tener múltiples entradas y una sola salida. Cada entrada es un número de 8 bits, y se asocia con un peso que indica su importancia en la salida final. En el caso de esta neurona, cuenta con 9 entradas numéricas de 8 bits, 4 de las cuales son números y las otras cuatro son los pesos asociados a dichos números. Además, se tiene un número  $\theta$  que se utiliza al final de la neurona para definir la salida. Cuando la suma de la multiplicación del peso asociado a un número con el número es menor a  $\theta$ , la salida es 0; en cambio, cuando esta suma es mayor o igual a  $\theta$ , la salida es 1. Es importante destacar que las neuronas artificiales son la base de las redes neuronales, y su complejidad aumenta a medida que se agregan más neuronas y conexiones entre ellas.

#### B. Especificaciones y restricciones:


- Entradas: 9 entradas de 8 bits
- $0 \leq \theta \leq 255$
- $\sum_{i=0}^{i=3} (\text{peso}_i * \text{numero}_i) \leq 255$
- Salida: 1 salida de 8 bits con valor decimal de 1 o 0



### 1.1.2 Símbolo

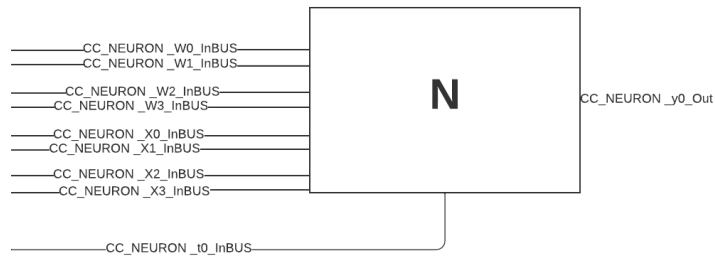

### 1.1.3 Diagrama caja negra

 

### 1.1.4 Funcionalidad



#### Ecuación característica

$$I \equiv CC\_SYSTEM\_y0\_Out \leq \sum_{i=0}^{i=3} (CC\_wi\_In * CC\_NEURON\_xi\_In) \geq CC\_NEURON\_t0\_In$$

or

$$0 \equiv CC\_SYSTEM\_y0\_Out \leq \sum_{i=0}^{i=3} (CC\_wi\_In * CC\_NEURON\_xi\_In) < CC\_NEURON\_t0\_In$$



#### Macro algoritmo

**Algorithm 1:** Neurona artificial**Data:**  $CC\_NEURON\_W0\_InBUS$  $,CC\_NEURON\_W1\_InBUS$  $,CC\_NEURON\_W2\_InBUS$  $,CC\_NEURON\_W3\_InBUS$  $,CC\_NEURON\_X0\_InBUS$  $,CC\_NEURON\_X1\_InBUS$  $,CC\_NEURON\_X2\_InBUS$  $,CC\_NEURON\_X3\_InBUS, CC\_NEURON\_t0\_InBUS)$ **Result:**  $CC\_NEURON\_y0\_Out$  (0, 1)

$$1 \equiv CC\_SYSTEM\_y0\_Out \leq \sum_{i=0}^{i=3} (CC\_wi\_In * CC\_NEURON\_xi\_In) \geq CC\_NEURON\_t0\_In$$

or

$$0 \equiv CC\_SYSTEM\_y0\_Out \leq \sum_{i=0}^{i=3} (CC\_wi\_In * CC\_NEURON\_xi\_In) < CC\_NEURON\_t0\_In$$

**1.1.5 HDL: Caja negra**

```
module BB_SYSTEM (
    //////////// OUTPUTS ////////////
    BB_SYSTEM_y0_Out,
    //////////// INPUTS ////////////
    BB_SYSTEM_t0_InBUS,
    BB_SYSTEM_x0_InBUS,
    BB_SYSTEM_w0_InBUS,
    BB_SYSTEM_x1_InBUS,
    BB_SYSTEM_w1_InBUS,
    BB_SYSTEM_x2_InBUS,
    BB_SYSTEM_w2_InBUS,
    BB_SYSTEM_x3_InBUS,
    BB_SYSTEM_w3_InBUS
);
//=====
// PARAMETER declarations
//=====
parameter NUMBER_DATAWIDTH = 8; // tamaño en terminos de bits
//=====
// PORT declarations
//=====
output BB_SYSTEM_y0_Out; //salida
input [NUMBER_DATAWIDTH-1:0] BB_SYSTEM_t0_InBUS; //theta
input [NUMBER_DATAWIDTH-1:0] BB_SYSTEM_x0_InBUS; // numero 0
input [NUMBER_DATAWIDTH-1:0] BB_SYSTEM_w0_InBUS; // peso numero 0
input [NUMBER_DATAWIDTH-1:0] BB_SYSTEM_x1_InBUS; // numero 1
input [NUMBER_DATAWIDTH-1:0] BB_SYSTEM_w1_InBUS; // peso numero 1
input [NUMBER_DATAWIDTH-1:0] BB_SYSTEM_x2_InBUS; // numero 2
input [NUMBER_DATAWIDTH-1:0] BB_SYSTEM_w2_InBUS; // peso numero 2
input [NUMBER_DATAWIDTH-1:0] BB_SYSTEM_x3_InBUS; // numero 3
input [NUMBER_DATAWIDTH-1:0] BB_SYSTEM_w3_InBUS; // peso numero 3
//=====
// REG/WIRE declarations
```



```
//=====

//=====
// Structural coding
//=====
CC_NEURON #(NUMBER_DATAWIDTH(NUMBER_DATAWIDTH)) CC_NEURON_u0 (
// port map - connection between master ports and signals/registers
.CC_NEURON_y0_Out(BB_SYSTEM_y0_Out),
.CC_NEURON_t0_InBUS(BB_SYSTEM_t0_InBUS),
.CC_NEURON_x0_InBUS(BB_SYSTEM_x0_InBUS),
.CC_NEURON_w0_InBUS(BB_SYSTEM_w0_InBUS),
.CC_NEURON_x1_InBUS(BB_SYSTEM_x1_InBUS),
.CC_NEURON_w1_InBUS(BB_SYSTEM_w1_InBUS),
.CC_NEURON_x2_InBUS(BB_SYSTEM_x2_InBUS),
.CC_NEURON_w2_InBUS(BB_SYSTEM_w2_InBUS),
.CC_NEURON_x3_InBUS(BB_SYSTEM_x3_InBUS),
.CC_NEURON_w3_InBUS(BB_SYSTEM_w3_InBUS)
);
endmodule
```

### 1.1.6 Definición vectores de prueba

En este caso como los existen muchos casos posibles, se ha seleccionado los siguientes casos para verificar la validez del programa:

#Prueba	t0	x0	w0	x1	w1	x2	w2	x3	w3	y0_out
0	0	0	0	0	0	0	0	0	0	1
1	1	0	0	0	0	0	0	0	0	0
2	40	1	1	2	2	3	3	4	4	0
3	128	0	0	0	0	0	0	0	0	0
4	1	1	1	0	0	0	0	0	0	1
5	2	1	1	2	2	3	3	4	4	1
6	255	1	1	2	2	3	3	4	4	0
7	1	1	0	100	2	100	0	55	1	1

Se consideró 6 casos para realizar las pruebas

- El primero para garantizar que cuando todos los valores son iguales el resultado debe ser igual a 1, ya que t0 no es mayor a la sumatoria de los números multiplicados por el peso.
- El segundo para garantizar que cuando t0 es mayor el resultado es igual a 0.
- El tercero para probar que t0 cuando t0 es mayor el resultado es igual a 0 solo que con números más variados.
- El quinto para confirmar que cuando dos números son iguales el resultado es igual a 0
- El sexto siendo caso contrario a la prueba 2 que debería ser igual a 1.
- Las pruebas 7ma y 8va tienen como fin comprobar que en efecto los números más grandes los reconoce la neurona que son con 255.

### 1.1.7 HDL: Vectores de prueba

```
module TB_SYSTEM();
// constants
// =====
// Parameter ( may differ for physical synthesis)
// =====
// general purpose registers
```





```
reg eachvec;
parameter NUMBER_DATAWIDTH = 8;
integer ii=0;

// test vector input registers
// =====
// INTERNAL WIRE AND REG DECLARATIONS
// =====
// wires (OUTPUTS)
wire TB_SYSTEM_y0_Out;
// reg (INPUTS)
reg [NUMBER_DATAWIDTH-1:0] TB_SYSTEM_t0_InBUS;
reg [NUMBER_DATAWIDTH-1:0] TB_SYSTEM_x0_InBUS;
reg [NUMBER_DATAWIDTH-1:0] TB_SYSTEM_w0_InBUS;
reg [NUMBER_DATAWIDTH-1:0] TB_SYSTEM_x1_InBUS;
reg [NUMBER_DATAWIDTH-1:0] TB_SYSTEM_w1_InBUS;
reg [NUMBER_DATAWIDTH-1:0] TB_SYSTEM_x2_InBUS;
reg [NUMBER_DATAWIDTH-1:0] TB_SYSTEM_w2_InBUS;
reg [NUMBER_DATAWIDTH-1:0] TB_SYSTEM_x3_InBUS;
reg [NUMBER_DATAWIDTH-1:0] TB_SYSTEM_w3_InBUS;

// assign statements (if any)
BB_SYSTEM BB_SYSTEM_u0 (
// port map - connection between master ports and signals/registers
.BB_SYSTEM_y0_Out(TB_SYSTEM_y0_Out),
.BB_SYSTEM_t0_InBUS(TB_SYSTEM_t0_InBUS),
.BB_SYSTEM_x0_InBUS(TB_SYSTEM_x0_InBUS),
.BB_SYSTEM_w0_InBUS(TB_SYSTEM_w0_InBUS),
.BB_SYSTEM_x1_InBUS(TB_SYSTEM_x1_InBUS),
.BB_SYSTEM_w1_InBUS(TB_SYSTEM_w1_InBUS),
.BB_SYSTEM_x2_InBUS(TB_SYSTEM_x2_InBUS),
.BB_SYSTEM_w2_InBUS(TB_SYSTEM_w2_InBUS),
.BB_SYSTEM_x3_InBUS(TB_SYSTEM_x3_InBUS),
.BB_SYSTEM_w3_InBUS(TB_SYSTEM_w3_InBUS)
);
initial
begin
// code that executes only once
// insert code here --> begin

// --> end
$display("Running testbench");
end
always
// optional sensitivity list
// @(event1 or event2 or .... eventn)

begin
// code executes for every event on sensitivity list
// insert code here --> begin
#10000 $monitor( "%1d:", ii, "Tiempo: %2d." , $time, "TB_SYSTEM_x0_InBUS = %b",
TB_SYSTEM_x0_InBUS, " | TB_SYSTEM_w0_InBUS= %b", TB_SYSTEM_w0_InBUS, " | TB_SYSTEM_y0_Out =
TB_SYSTEM_y0_Out);

#0 TB_SYSTEM_t0_InBUS <= 0; TB_SYSTEM_x0_InBUS <= 0; TB_SYSTEM_w0_InBUS <= 0; TB_SYSTEM_x1_InBUS
```



```
TB_SYSTEM_x2_InBUS <= 0; TB_SYSTEM_w2_InBUS <= 0;
TB_SYSTEM_x3_InBUS <= 0; TB_SYSTEM_w3_InBUS <= 0; // CHECK 1

#20000 TB_SYSTEM_t0_InBUS <= 1; TB_SYSTEM_x0_InBUS <= 0; TB_SYSTEM_w0_InBUS <= 0;
TB_SYSTEM_x1_InBUS <= 0; TB_SYSTEM_w1_InBUS <= 0;
TB_SYSTEM_x2_InBUS <= 0; TB_SYSTEM_w2_InBUS <= 0;
TB_SYSTEM_x3_InBUS <= 0; TB_SYSTEM_w3_InBUS <= 0; // CHECK 0

#20000 TB_SYSTEM_t0_InBUS <= 40; TB_SYSTEM_x0_InBUS <= 1; TB_SYSTEM_w0_InBUS <= 1;
TB_SYSTEM_x1_InBUS <= 2; TB_SYSTEM_w1_InBUS <= 2;
TB_SYSTEM_x2_InBUS <= 3; TB_SYSTEM_w2_InBUS <= 3;
TB_SYSTEM_x3_InBUS <= 4; TB_SYSTEM_w3_InBUS <= 4; // CHECK 0

#20000 TB_SYSTEM_t0_InBUS <= 128; TB_SYSTEM_x0_InBUS <= 0; TB_SYSTEM_w0_InBUS <= 0;
TB_SYSTEM_x1_InBUS <= 0; TB_SYSTEM_w1_InBUS <= 0;
TB_SYSTEM_x2_InBUS <= 0; TB_SYSTEM_w2_InBUS <= 0;
TB_SYSTEM_x3_InBUS <= 0; TB_SYSTEM_w3_InBUS <= 0; // CHECK 0

#20000 TB_SYSTEM_t0_InBUS <= 1; TB_SYSTEM_x0_InBUS <= 1; TB_SYSTEM_w0_InBUS <= 1;
TB_SYSTEM_x1_InBUS <= 0; TB_SYSTEM_w1_InBUS <= 0;
TB_SYSTEM_x2_InBUS <= 0; TB_SYSTEM_w2_InBUS <= 0;
TB_SYSTEM_x3_InBUS <= 0; TB_SYSTEM_w3_InBUS <= 0; // CHECK 1

#20000 TB_SYSTEM_t0_InBUS <= 2; TB_SYSTEM_x0_InBUS <= 1; TB_SYSTEM_w0_InBUS <= 1;
TB_SYSTEM_x1_InBUS <= 2; TB_SYSTEM_w1_InBUS <= 2;
TB_SYSTEM_x2_InBUS <= 3; TB_SYSTEM_w2_InBUS <= 3;
TB_SYSTEM_x3_InBUS <= 4; TB_SYSTEM_w3_InBUS <= 4; // CHECK 1


#20000 TB_SYSTEM_t0_InBUS <= 255; TB_SYSTEM_x0_InBUS <= 1; TB_SYSTEM_w0_InBUS <= 1;
TB_SYSTEM_x1_InBUS <= 2; TB_SYSTEM_w1_InBUS <= 2;
TB_SYSTEM_x2_InBUS <= 3; TB_SYSTEM_w2_InBUS <= 3;
TB_SYSTEM_x3_InBUS <= 4; TB_SYSTEM_w3_InBUS <= 4; // CHECK 1

#20000 TB_SYSTEM_t0_InBUS <= 1; TB_SYSTEM_x0_InBUS <= 1; TB_SYSTEM_w0_InBUS <= 0;
TB_SYSTEM_x1_InBUS <= 100; TB_SYSTEM_w1_InBUS <= 2;
TB_SYSTEM_x2_InBUS <= 100; TB_SYSTEM_w2_InBUS <= 0;
TB_SYSTEM_x3_InBUS <= 55; TB_SYSTEM_w3_InBUS <= 1; // CHECK 1

@eachvec;
$finish;
// --> end
end
endmodule
```
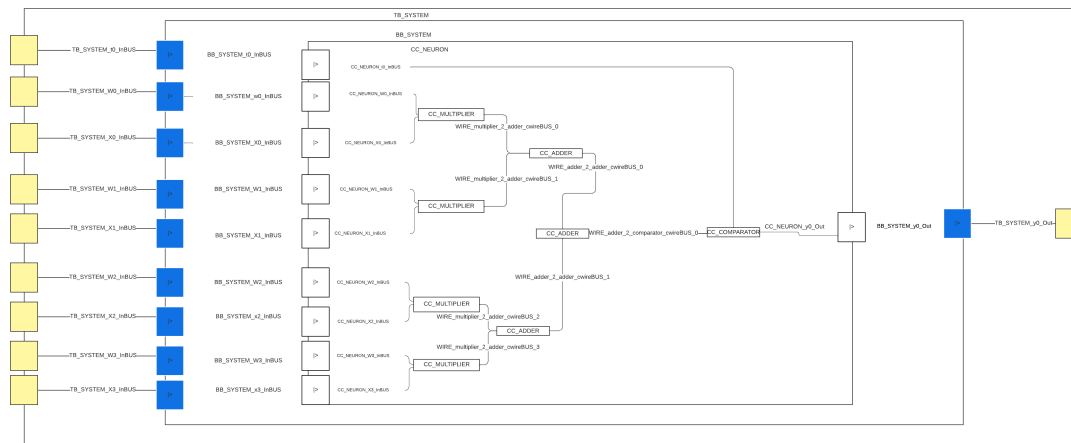
### 1.1.8 Diagrama caja blanca

En este caso el diagrama corresponde solamente a la neurona.



En el diagrama se puede ver los componentes necesarios para completar una neurona, la multiplicación entre numero y peso, La sumatoria resultado de estas multiplicaciones para así llegar finalizar con una comparación con con  $t_0$  y evidenciar una respuesta (1 o 0). El diagrama muestra en detalle los cables con respectivos nombres para llegar a este componente.

### 1.1.9 HDL: Caja blanca

```
module CC_NEURON (  
  //////////// OUTPUTS ///////////  
  CC_NEURON_y0_Out,  
  //////////// INPUTS ///////////  
  CC_NEURON_t0_InBUS,  
  CC_NEURON_x0_InBUS,  
  CC_NEURON_w0_InBUS,  
  CC_NEURON_x1_InBUS,  
  CC_NEURON_w1_InBUS,  
  CC_NEURON_x2_InBUS,  
  CC_NEURON_w2_InBUS,  
  CC_NEURON_x3_InBUS,  
  CC_NEURON_w3_InBUS  
);  
//=====
```

```
// PARAMETER declarations  
//=====
```

```
parameter NUMBER_DATAWIDTH = 8;  
//=====
```

```
// PORT declarations  
//=====
```

```
output  CC_NEURON_y0_Out;  
input   [NUMBER_DATAWIDTH-1:0] CC_NEURON_t0_InBUS; //coeficiente o  
input   [NUMBER_DATAWIDTH-1:0] CC_NEURON_x0_InBUS;  
input   [NUMBER_DATAWIDTH-1:0] CC_NEURON_w0_InBUS;  
input   [NUMBER_DATAWIDTH-1:0] CC_NEURON_x1_InBUS;  
input   [NUMBER_DATAWIDTH-1:0] CC_NEURON_w1_InBUS;  
input   [NUMBER_DATAWIDTH-1:0] CC_NEURON_x2_InBUS;  
input   [NUMBER_DATAWIDTH-1:0] CC_NEURON_w2_InBUS;  
input   [NUMBER_DATAWIDTH-1:0] CC_NEURON_x3_InBUS;  
input   [NUMBER_DATAWIDTH-1:0] CC_NEURON_w3_InBUS;  
  
//=====
```



```
// REG/WIRE declarations
//=====
wire [NUMBER_DATAWIDTH-1:0] WIRE_multiplier_2_adder_cwireBUS_0;
wire [NUMBER_DATAWIDTH-1:0] WIRE_multiplier_2_adder_cwireBUS_1;
wire [NUMBER_DATAWIDTH-1:0] WIRE_multiplier_2_adder_cwireBUS_2;
wire [NUMBER_DATAWIDTH-1:0] WIRE_multiplier_2_adder_cwireBUS_3;

wire [NUMBER_DATAWIDTH-1:0] WIRE_adder_2_adder_cwireBUS_0;
wire [NUMBER_DATAWIDTH-1:0] WIRE_adder_2_adder_cwireBUS_1;

wire [NUMBER_DATAWIDTH-1:0] WIRE_adder_2_comparator_cwireBUS_0;

//=====
// Structural coding
//=====
//STRUCTURAL
CC_MULTIPLIER CC_MULTIPLIER_u0 (// instanciación multiplier x0 y w0
// port map - connection between master ports and signals/registers
.CC_MULTIPLIER_product_Out(WIRE_multiplier_2_adder_cwireBUS_0),
.CC_MULTIPLIER_m0_InBUS(CC_NEURON_x0_InBUS),
.CC_MULTIPLIER_m1_InBUS(CC_NEURON_w0_InBUS)
);

CC_MULTIPLIER CC_MULTIPLIER_u1 (// instanciación multiplier x1 y w1
// port map - connection between master ports and signals/registers
.CC_MULTIPLIER_product_Out(WIRE_multiplier_2_adder_cwireBUS_1),
.CC_MULTIPLIER_m0_InBUS(CC_NEURON_x1_InBUS),
.CC_MULTIPLIER_m1_InBUS(CC_NEURON_w1_InBUS)
);

CC_MULTIPLIER CC_MULTIPLIER_u2 (// instanciación multiplier x2 y w2
// port map - connection between master ports and signals/registers
.CC_MULTIPLIER_product_Out(WIRE_multiplier_2_adder_cwireBUS_2),
.CC_MULTIPLIER_m0_InBUS(CC_NEURON_x2_InBUS),
.CC_MULTIPLIER_m1_InBUS(CC_NEURON_w2_InBUS)
);

CC_MULTIPLIER CC_MULTIPLIER_u3 (//// instanciación multiplier x3 y w3
// port map - connection between master ports and signals/registers
.CC_MULTIPLIER_product_Out(WIRE_multiplier_2_adder_cwireBUS_3),
.CC_MULTIPLIER_m0_InBUS(CC_NEURON_x3_InBUS),
.CC_MULTIPLIER_m1_InBUS(CC_NEURON_w3_InBUS)
);

CC_ADDER CC_ADDER_u0 (// sumatoria x0*w0 + x1*w1
// port map - connection between master ports and signals/registers
.CC_ADDER_sum_Out(WIRE_adder_2_adder_cwireBUS_0),
.CC_ADDER_a0_InBUS(WIRE_multiplier_2_adder_cwireBUS_0),
.CC_ADDER_a1_InBUS(WIRE_multiplier_2_adder_cwireBUS_1)
);

CC_ADDER CC_ADDER_u1 (// sumatoria x2*w2 + x3*w3
```



```
// port map - connection between master ports and signals/registers
.CC_ADDER_sum_Out(WIRE_adder_2_adder_cwireBUS_1),
.CC_ADDER_a0_InBUS(WIRE_multiplier_2_adder_cwireBUS_2),
.CC_ADDER_a1_InBUS(WIRE_multiplier_2_adder_cwireBUS_3)

);

CC_ADDER CC_ADDER_u2 (// sumatoria  $x0*w0 + x1*w1 + x2*w2 + x3*w3$ 
// port map - connection between master ports and signals/registers
.CC_ADDER_sum_Out(WIRE_adder_2_comparator_cwireBUS_0),
.CC_ADDER_a0_InBUS(WIRE_adder_2_adder_cwireBUS_1),
.CC_ADDER_a1_InBUS(WIRE_adder_2_adder_cwireBUS_0)

);

CC_COMPARATOR CC_COMPARATOR_u2 (
//  $(x0*w0 + x1*w1 + x2*w2 + x3*w3) > t0 \Rightarrow 0$  ||
//  $(x0*w0 + x1*w1 + x2*w2 + x3*w3) \leq t0 \Rightarrow 1$ 

// port map - connection between master ports and signals/registers
.CC_COMPARATOR_result_Out (CC_NEURON_y0_Out),
.CC_COMPARATOR_c0_InBUS(CC_NEURON_t0_InBUS),
.CC_COMPARATOR_c1_InBUS(WIRE_adder_2_comparator_cwireBUS_0)

);

endmodule
```

### 1.1.10 HDL: bloques

**Para los bloques ADDER u0, u1 y u2 sus codigos corresponden al siguiente:**

```
module CC_ADDER (
////////// OUTPUTS //////////
CC_ADDER_sum_Out,
////////// INPUTS //////////
CC_ADDER_a0_InBUS,
CC_ADDER_a1_InBUS
);
//=====
// PARAMETER declarations
//=====
parameter NUMBER_DATAWIDTH = 8;
//=====
// PORT declarations
//=====
output [NUMBER_DATAWIDTH-1:0] CC_ADDER_sum_Out;
input [NUMBER_DATAWIDTH-1:0] CC_ADDER_a0_InBUS;
input [NUMBER_DATAWIDTH-1:0] CC_ADDER_a1_InBUS;
//=====
// REG/WIRE declarations
//=====

//=====
```



```
// Structural coding
//=====

assign CC_ADDER_sum_Out= CC_ADDER_a0_InBUS + CC_ADDER_a1_InBUS;

endmodule
```

**Para el bloque COMPARATOR su código corresponde al siguiente:**

```
module CC_COMPARATOR (
////////// OUTPUTS //////////
CC_COMPARATOR_result_Out,
////////// INPUTS //////////
CC_COMPARATOR_c0_InBUS,
CC_COMPARATOR_c1_InBUS
);
//=====
// PARAMETER declarations
//=====
parameter NUMBER_DATAWIDTH = 8;
//=====
// PORT declarations
//=====
output reg CC_COMPARATOR_result_Out;
input [NUMBER_DATAWIDTH-1:0] CC_COMPARATOR_c0_InBUS;
input [NUMBER_DATAWIDTH-1:0] CC_COMPARATOR_c1_InBUS;
//=====
// REG/WIRE declarations
//=====

//=====
// Structural coding
//=====
always @(*) begin

if (CC_COMPARATOR_c0_InBUS>CC_COMPARATOR_c1_InBUS) begin
CC_COMPARATOR_result_Out = 0;
end else begin
CC_COMPARATOR_result_Out = 1;
end
end

endmodule
```

**Para los bloques MULTIPLIER u0, u1 y u2 sus códigos corresponden al siguiente:**

```
module CC_MULTIPLIER (
////////// OUTPUTS //////////
CC_MULTIPLIER_product_Out,
////////// INPUTS //////////
CC_MULTIPLIER_m0_InBUS,
CC_MULTIPLIER_m1_InBUS
);
```



```
//=====
//  PARAMETER declarations
//=====
parameter NUMBER_DATAWIDTH = 8;
//=====
//  PORT declarations
//=====
output  [NUMBER_DATAWIDTH-1:0] CC_MULTIPLIER_product_Out;
input   [NUMBER_DATAWIDTH-1:0] CC_MULTIPLIER_m0_InBUS;
input   [NUMBER_DATAWIDTH-1:0] CC_MULTIPLIER_m1_InBUS;
//=====
//  REG/WIRE declarations
//=====

//=====
//  Structural coding
//=====

assign CC_MULTIPLIER_product_Out = CC_MULTIPLIER_m0_InBUS * CC_MULTIPLIER_m1_InBUS;


endmodule
```

### 1.1.11 Simulación temporal


A continuación se presenta un diagrama de lo que se espera obtener del sistema. Cabe resaltar que el orden de las pruebas es igual como se muestra en la tabla con los vectores de prueba como se ve a continuación:

#Prueba	t0	x0	w0	x1	w1	x2	w2	x3	w3	y0_out
0	0	0	0	0	0	0	0	0	0	1
1	1	0	0	0	0	0	0	0	0	0
2	40	1	1	2	2	3	3	4	4	0
3	128	0	0	0	0	0	0	0	0	0
4	1	1	1	0	0	0	0	0	0	1
5	2	1	1	2	2	3	3	4	4	1
6	255	1	1	2	2	3	3	4	4	0
7	1	1	0	100	2	100	0	55	1	1

 
Por lo que resultados de la simulación debería verse de la siguiente manera:



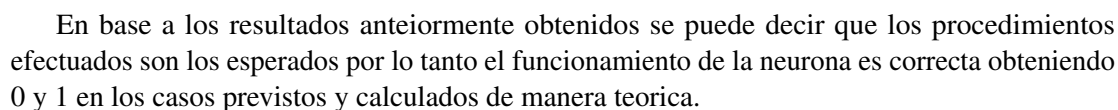
El siguiente diagrama de tiempos obtenido en la herramienta Quartus de Altera. Se puede ver los resultados de la simulación:



### 1.1.12 Diagramas QUARTUS

 



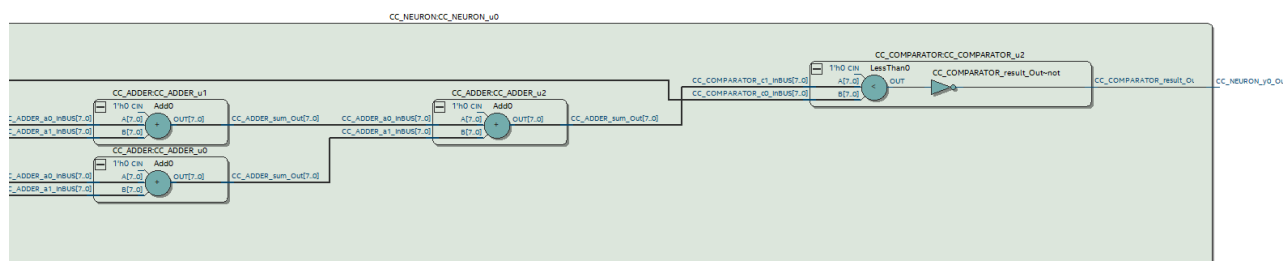

Vista cercana de los componentes adder y comparar de CC\_Neuron

### 1.1.13 Resultados y lecciones aprendidas

Después de realizar la práctica utilizando el programa Quartus y la manipulación de diversos códigos en Verilog para el desarrollo de una neurona artificial, se puede concluir que se ha logrado comprender los elementos básicos de las redes neuronales y su funcionamiento. La neurona artificial es un elemento simple pero importante en la construcción de redes neuronales, ya que es la base para la creación de capas y redes más complejas. La práctica permitió entender cómo funciona una neurona artificial y cómo los valores y parámetros de entrada influyen en la salida final de la neurona. Se logró implementar una neurona artificial en Quartus que cumple con los criterios establecidos. La práctica también permitió adquirir conocimientos prácticos y aplicados sobre el lenguaje Verilog, lo cual puede ser de gran utilidad en futuros proyectos que involucren el desarrollo de hardware digital.